

Paper ID:

3	0	0	6
---	---	---	---

Roll No.

--	--	--	--	--	--	--	--	--	--

B TECH
(SEM III) THEORY EXAMINATION 2017-18
NETWORK ANALYSIS AND SYNTHESIS

Time: 3Hours


Max. Marks: 100

Note: Attempt all Sections.

SECTION A

1. Attempt all questions in brief. 2 x 10 = 20

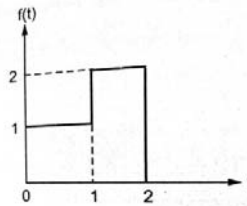a) Determine the function for the given waveform-




- b) Write the properties of LC driving point function?
- c) What are the different types of network function?
- d) What is the condition for Symmetry of y-parameter and t-parameter?
- e) What are the properties of Hurwitz polynomial?
- f) Draw the waveform represented by the following function-
 $f_1(t) = (t-1)u(t-1)$ (ii) $f_2(t) = tu(t+T)$
- g) Write down the statement for Maximum power transfer theorem with example?
- h) Write the Y-parameter in terms of h-parameter?
- i) What do you mean by incidence matrix and reduced incidence matrix?
- j) Define network analysis and network synthesis.

SECTION B

2. Attempt any three of the following: 10 x 3 = 30

a) Draw pole-zero plot of the given network function $V(s) = \frac{10s}{(s+3)(s+2)}$ and obtain v(t) with the help of pole-zero plot?

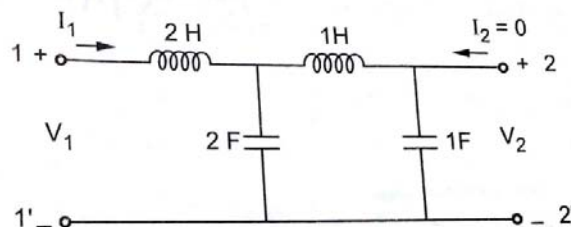
b) Obtain $\frac{V_2}{I_1}$ and $\frac{V_2}{V_1}$ for the given network-



c) Obtain the Foster forms for the given network-

$$Z(s) = \frac{(s+1)(s+3)}{(s+2)(s+4)}$$

d) Find the Y-parameter for the network-

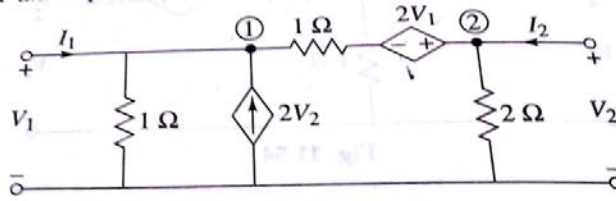

e) Test given function F(s) for positive realness?


$$F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$$

SECTION C


3. Attempt any *one* part of the following:

10 x 1 = 10

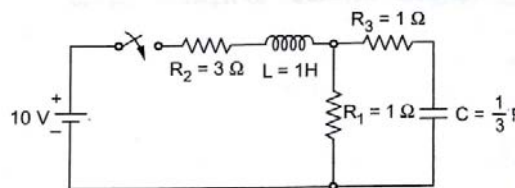
a) Calculate the current flowing through the branch containing resistance R1 in given network using Thevenin theorem



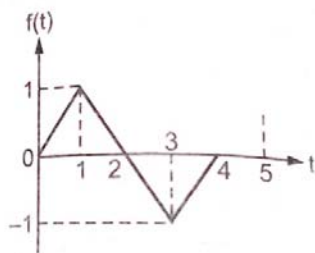b) Write the expression for the waveform shown in the figure-



(i)

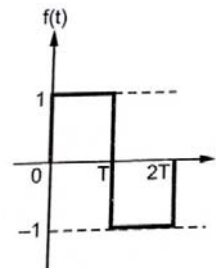


(ii)


4. Attempt any *one* part of the following:

10 x 1 = 10

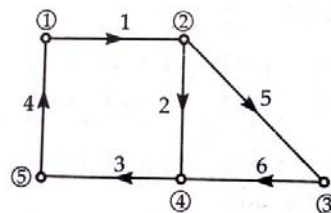a) Show the cut-set for the graph for the given network and develop the fundamental cut-set matrix-



b) Find the T-parameter using the concept of interconnection of two given network-

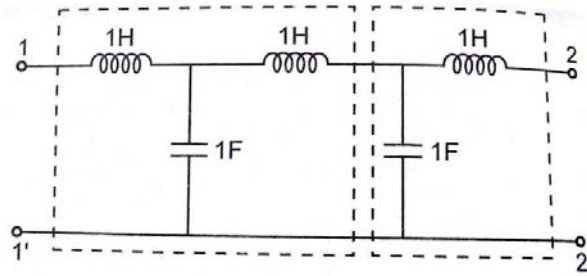

5. Attempt any one part of the following:

10 x 1 = 10

a) What are the properties of Positive real function? Test whether the polynomial is Hurwitz or not? $F(s) = s^3 + 4s^2 + 5s + 20$


b) Realize the Caer forms of the following impedance function-

$$Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$


6. Attempt any one part of the following:

10 x 1 = 10

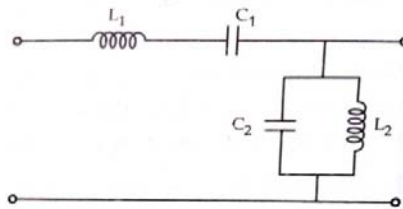a) Define the zeros of transmission? Identify the zeros of transmission of the given network-




b) Determine the Z-parameter for the given network?

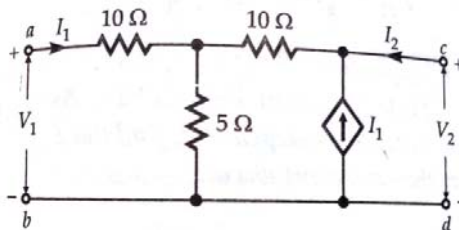

7. Attempt any one part of the following:

10 x 1 = 10

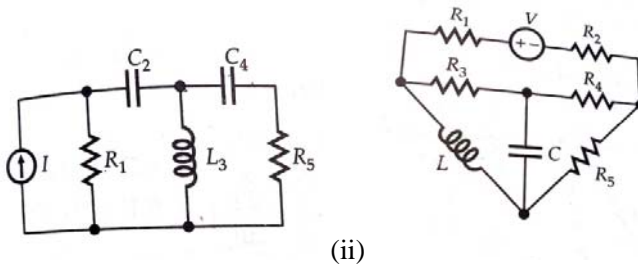a) Draw the dual of the network shown in the figure-



b) Discuss the Non-inverting VCCS and CCVS circuit?